

# ECE3084-L16 S-domain Circuit Analysis


Tuesday, April 4, 2017 5:04 AM

## Example:

$$\text{Input} = v(t) \quad \text{Output} = i(t)$$

$$\text{KVL: } v(t) = v_R(t) + v_L(t)$$

$$v(t) = R i(t) + L \frac{di(t)}{dt}$$

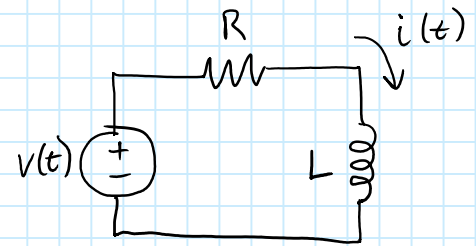

$$\text{Take LT: } V(s) = R I(s) + s L I(s) - L i(0)$$

$$(sL + R) I(s) = V(s) + L i(0)$$

Standard form has  
coef of 1 on highest  
power of s.

$$\left(s + \frac{R}{L}\right) I(s) = \frac{1}{L} V(s) + i(0)$$

$$I(s) = \frac{1/L}{s + R/L} V(s) + \frac{i(0)}{s + R/L}$$

$$i(t) = \underbrace{\mathcal{L}^{-1} \left[ \frac{1/L}{s + R/L} V(s) \right]}_{\text{Forced response due to input } v(t)} + \underbrace{i(0) e^{-\frac{R}{L} t}}_{\text{Natural response due to init conds}}$$

$$\text{Time Constant? } \tau = \frac{L}{R} \quad \left( t = \frac{L}{R} \text{ gives an } e^{-1} \text{ term} \right)$$

Transfer function? Set init conds to 0 and find  $\frac{\text{Output}(s)}{\text{Input}(s)}$

$$H(s) = \frac{1/L}{s + R/L}$$

$$\text{High or low pass? } H(j\infty) = 0 \quad \text{Low}$$

$$\text{Pass band gain? } H(j0) = \frac{1}{R} \quad \text{Because we input voltage, but measure current.}$$

What if we looked at other outputs?

$$v_R(t) \Rightarrow \text{Low pass}$$


$$v_L(t) \Rightarrow \text{High pass}$$

## Series RLC:

Lots of options for the output:

$i(t)$ , Band Pass	$V_R(t)$ , Band Pass	$V_L(t)$ , High pass	$V_C(t)$ , Low Pass	$V_{LC}(t)$ , Notch Filter
--------------------------	----------------------------	----------------------------	---------------------------	----------------------------------

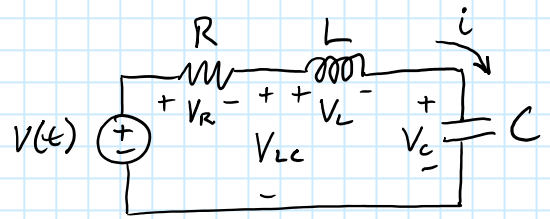↳  $i(t) = \frac{1}{R} V_R(t)$  same filter, different gain



For output  $V_C(t)$ :

$$\text{KVL: } V(t) = R i(t) + L \frac{di(t)}{dt} + V_C(t)$$

$$\text{Plug in } i(t) = C \frac{dV_C(t)}{dt}$$

$$V(t) = RC \frac{dV_C(t)}{dt} + LC \frac{d^2 V_C(t)}{dt^2} + V_C(t)$$

$$LC \ddot{V}_C + RC \dot{V}_C + V_C = V(t) \quad \text{Take LT}$$

$$LC s^2 V_C(s) - LC s V_C(0) - LC \dot{V}_C(0) + RC (s V_C(s) - RC V_C(0)) + V_C(s) = V(s)$$

$$(LC s^2 + RC s + 1) V_C(s) = V(s) + LC s V_C(0) + LC \dot{V}_C(0) + RC V_C(0)$$

$$\left(s^2 + \frac{R}{L} s + \frac{1}{LC}\right) V_C(s) = \frac{1}{LC} V(s) + s V_C(0) + \dot{V}_C(0) + \frac{R}{L} V_C(0)$$

$$V_C(s) = \underbrace{\frac{1/LC}{s^2 + \frac{R}{L} s + \frac{1}{LC}}}_{H(s)} V(s) + \frac{s V_C(0) + \dot{V}_C(0) + \frac{R}{L} V_C(0)}{s^2 + \frac{R}{L} s + \frac{1}{LC}}$$

$H(s)$   
Transfer Function

Is there an easier way?

Recall: For phasors, complex impedances made it easier to set things up — could treat everything like a resistor.

Do you know where the phasor domain impedance formulas come from?

Impedance is the voltage-current ratio  $\frac{V}{I}$  for a component, assuming all initial conditions are zero.

## Resistors

$$\text{Time domain: } V(t) = R i(t)$$

$$\text{Fourier domain: } V(j\omega) = R I(j\omega) \quad Z_R = \frac{V(j\omega)}{I(j\omega)} = R$$

$$s\text{-domain: } V(s) = R I(s) \quad Z_R = \frac{V(s)}{I(s)} = R$$

# Capacitor

Time Domain:  $i_c(t) = C \frac{dv_c(t)}{dt}$

Fourier Domain:  $I_c(j\omega) = j\omega C V_c(j\omega)$        $Z_c(j\omega) = \frac{V_c(j\omega)}{I_c(j\omega)} = \frac{1}{j\omega C}$

s-domain:  $I_c(s) = sC V_c(s) - C v_c(0^-)$

$$sC V_c(s) = I_c(s) + C v_c(0^-)$$

$$V_c(s) = \underbrace{\frac{1}{sC}}_{\text{"Transfer Function"}} I_c(s) + \underbrace{\frac{v_c(0^-)}{s}}_{\text{From initial conditions. Deal with separately}}$$

"Transfer Function"  
Assumes init conds  
are all zero.

From initial conditions.  
Deal with separately

$$Z_c(s) = \left. \frac{V_c(s)}{I_c(s)} \right|_{v_c(0^-)=0} = \frac{1}{sC}$$

Can view the initial condition as either a voltage source or a current source in the s-domain:


$$V_c(s) = Z_c(s) I_c(s) + \frac{v_c(0^-)}{s}$$

Total  
voltage  
across  
the  
model

Voltage  
across  
 $Z_c(s) = \frac{1}{sC}$

s-domain  
voltage  
source

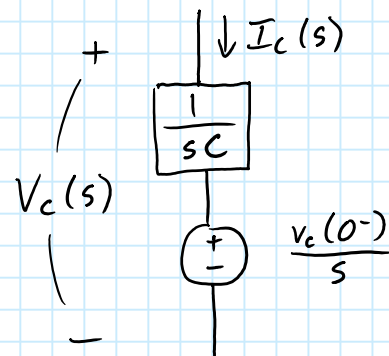(Transforms to a step fn,  
i.e. the cap just holds  
the voltage absent  
anything else happening.)



$$I_c(s) = sC V(s) - C v_c(0^-) \quad (\text{From before})$$

$$I_c(s) = \frac{1}{Z_c(s)} V(s) - C v_c(0^-)$$


$$\frac{1}{Z_c(s)} V(s) = I_c(s) + C v_c(0^-)$$

Current  
through  
 $Z_c(s) = \frac{1}{sC}$

Total  
current  
into the  
model

s-domain  
current  
supply

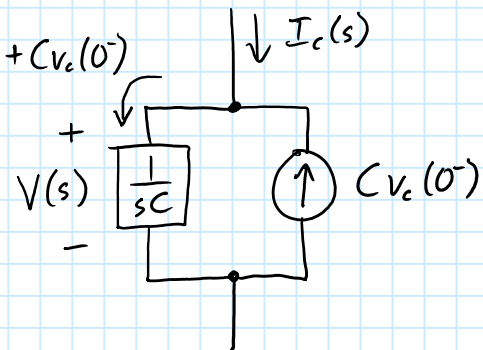(Transforms to a  $\delta$  fn,  
i.e. an impulse of current  
that sets the cap to its  
initial voltage, then no  
more current absent  
anything else happening.)



# Inductor

Time domain:  $v_L(t) = L \frac{di_L(t)}{dt}$


Fourier domain:  $V_L(j\omega) = j\omega L I_L(j\omega) \quad Z_L(j\omega) = \frac{V_L(j\omega)}{I_L(j\omega)} = j\omega L$

s-domain:  $V_L(s) = \underbrace{sL I_L(s)}_{\text{"Transfer function"}} - \underbrace{L i_L(0^-)}_{\text{Due to init conditions}}$

$$Z_L(s) = \frac{V_L(s)}{I_L(s)} \Big|_{i_L(0^-)=0} = sL$$

Can handle init cond w/ voltage or current supply:
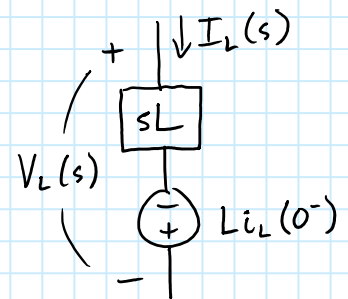
$$\underbrace{V_L(s)}_{\text{Total voltage across model}} = \underbrace{Z_L(s) I_L(s)}_{\text{Voltage across } Z_L(s)=sL} - \underbrace{L i_L(0^-)}_{\substack{\text{s-domain voltage source} \\ \text{(Transforms to an impulse of voltage to instantaneously set the appropriate initial current.)}}}$$





Solve for current:

$$I_L(s) = \frac{1}{sL} V_L(s) + \frac{L i_L(0^-)}{sL}$$

$$I_L(s) = \frac{1}{Z_L} V_L(s) + \frac{i_L(0^-)}{s}$$
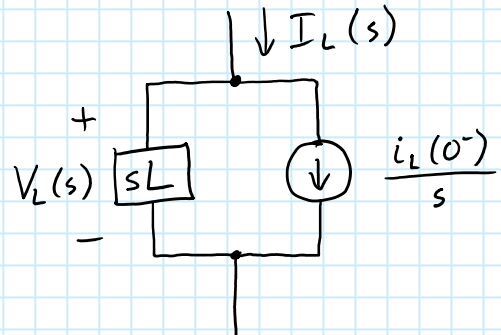
$$\underbrace{I_L(s)}_{\text{Current through entire model}} = \underbrace{\frac{1}{Z_L} V_L(s)}_{\text{Current through } Z_L(s)=sL} + \underbrace{\frac{i_L(0^-)}{s}}_{\substack{\text{s-domain current source} \\ \text{(transforms to a time domain step function - the inductor "holds" the current absent other influences.)}}}$$



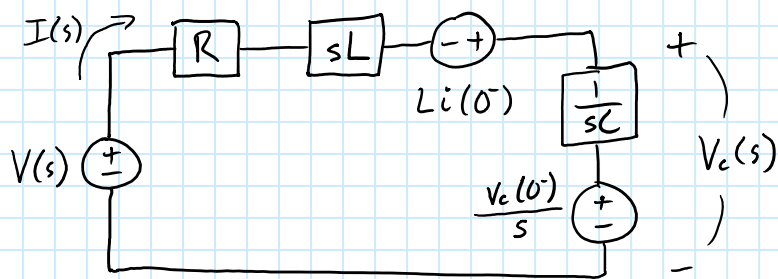

$$i = C \frac{dV_c}{dt}$$

$$i(0^-) = C \dot{v}_c(0^-)$$

Voltage divider: 
$$V_c(s) - \frac{V_c(0^-)}{s} = \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} \left( V(s) + Li(0^-) - \frac{V_c(0^-)}{s} \right)$$

$$V_c(s) = \frac{\frac{1}{sC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} V(s) + \frac{\frac{1}{C} i(0^-) - \frac{1}{sC} V_c(0^-)}{s^2 + \frac{R}{L}s + \frac{1}{LC}} + \frac{V_c(0^-)}{s}$$

$$= H(s) V(s) + \frac{\frac{s}{C} i(0^-) - \frac{1}{sC} V_c(0^-) + (s^2 + \frac{R}{L}s + \frac{1}{sC}) V_c(0^-)}{s(s^2 + \frac{R}{L}s + \frac{1}{LC})}$$

Plug in  $i = C \frac{dV_c}{dt} \Rightarrow i(0^-) = C \dot{v}_c(0^-)$


$$= H(s) V(s) + \frac{\dot{v}_c(0^-) + s V_c(0^-) + \frac{R}{L} V_c(0^-)}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Same transfer function & init conds terms as before.

Transfer function is easy to get

b/c you can ignore init conds:

Just a voltage divider

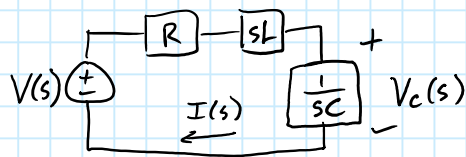


$$V_c(s) = \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} V(s) \left( \frac{\frac{s}{L}}{\frac{s}{L}} \right) = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} V(s)$$

$$V_R(s) = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}} V(s) \quad I(s) = \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}} V(s)$$

$$V_L(s) = \frac{s^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}} V(s) \quad V_{LC}(s) = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} V(s)$$

Example: Find  $i_L(t)$

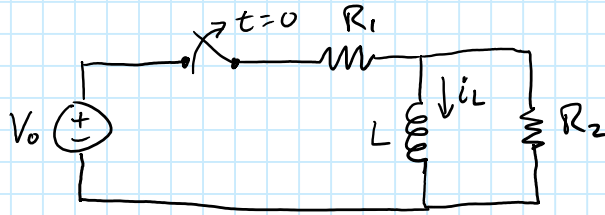

$$i_L(0^-) = \frac{V_0}{R_1}$$

$$I_L(s) = \frac{L i_L(0^-)}{R_2 + sL} = \frac{L (V_0/R_1)}{sL + R_2} = \frac{V_0/R_1}{s + R_2/L}$$

$$i(t) = \frac{V_0}{R_1} e^{-\frac{R_2}{L}t} u(t) \quad \text{Time constant } \tau = \frac{L}{R_2}$$

After switch opens:

